



**North South University**  
Department of Electrical & Computer Engineering

**PROJECT REPORT**

Course Code: *CSE231L*

Course Title: *Digital Logic Design Lab*

Section: *04*

Project Name:

*Display “CSE231-9” in  
7 Segment Display*

Date of Submission: *April, 2022*

Submitted by Group Number: *09*

Group members:

1. *Zobaer Ahammad Zamil, ID: 2021796642*
2. *Al Nahian Niloy, ID: 2031445642*
3. *Osmita Monzur Subonty, ID: 2011708642*


Course Instructor: Md. Shahriar Hussain (HSM)

Submitted To: Md. Anisur Rahman Asif

We have to print "CSE231-9" in 7 segment display. Here is the truth table for it, where A, B, C will be input and, a, b, c, d, e, f, g will be output.


Truth Table :

A	B	C	a	b	c	d	e	f	g	output
0	0	0	1	0	0	1	1	1	0	C
0	0	1	1	0	1	1	0	1	1	S
0	1	0	1	0	0	1	1	1	1	E
0	1	1	1	1	0	1	1	0	1	Z
1	0	0	1	1	1	1	0	0	1	3
1	0	1	0	1	1	0	0	0	0	1
1	1	0	0	0	0	0	0	0	1	-
1	1	1	1	1	1	1	0	1	1	9

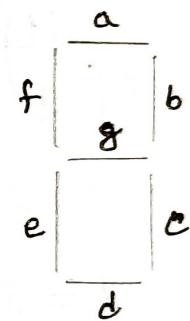


7 segment  
display

K-maps :

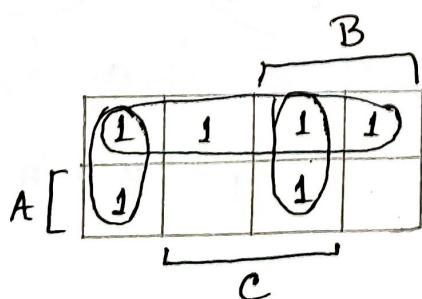


[for  $\rightarrow a$ ]


$$a = \underline{1} + \bar{A} + BC + \bar{B}\bar{C}$$

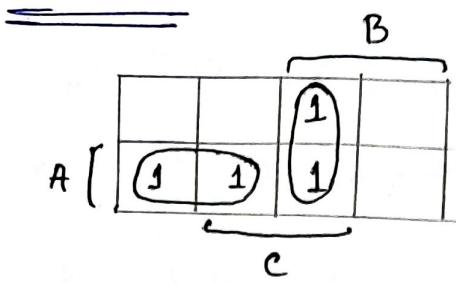For  $b$ :


$$b = A\bar{B} + Bc$$

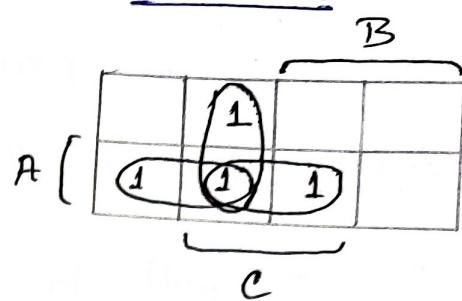For  $c$ :


$$c = A\bar{B} + Ac + \bar{B}c$$

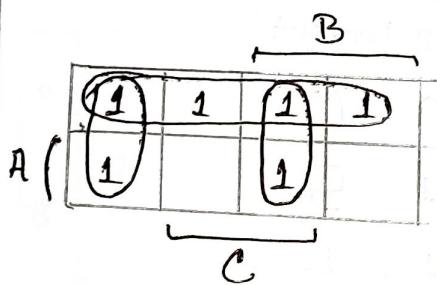For  $d$ :


$$d = \bar{A} + Bc + \bar{B}\bar{c}$$

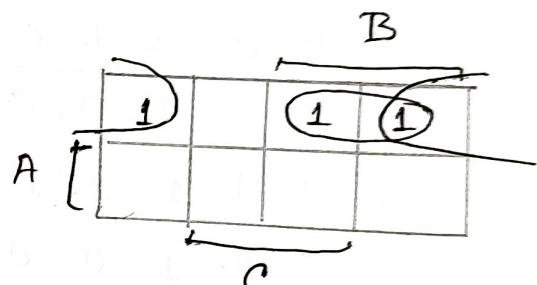For  $e$ :


$$e = \bar{A}B + \bar{A}\bar{C}$$

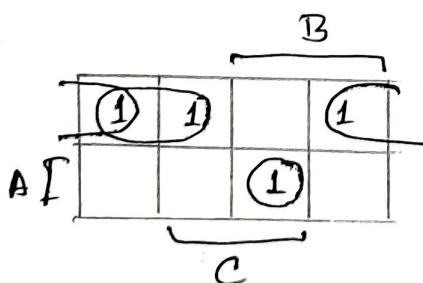For  $f$ :

$$f = ABC + \bar{A}\bar{B} + \bar{A}\bar{C}$$

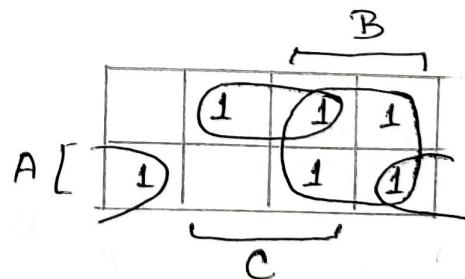For  $g$ :

$$g = B + \bar{A}C + AC$$

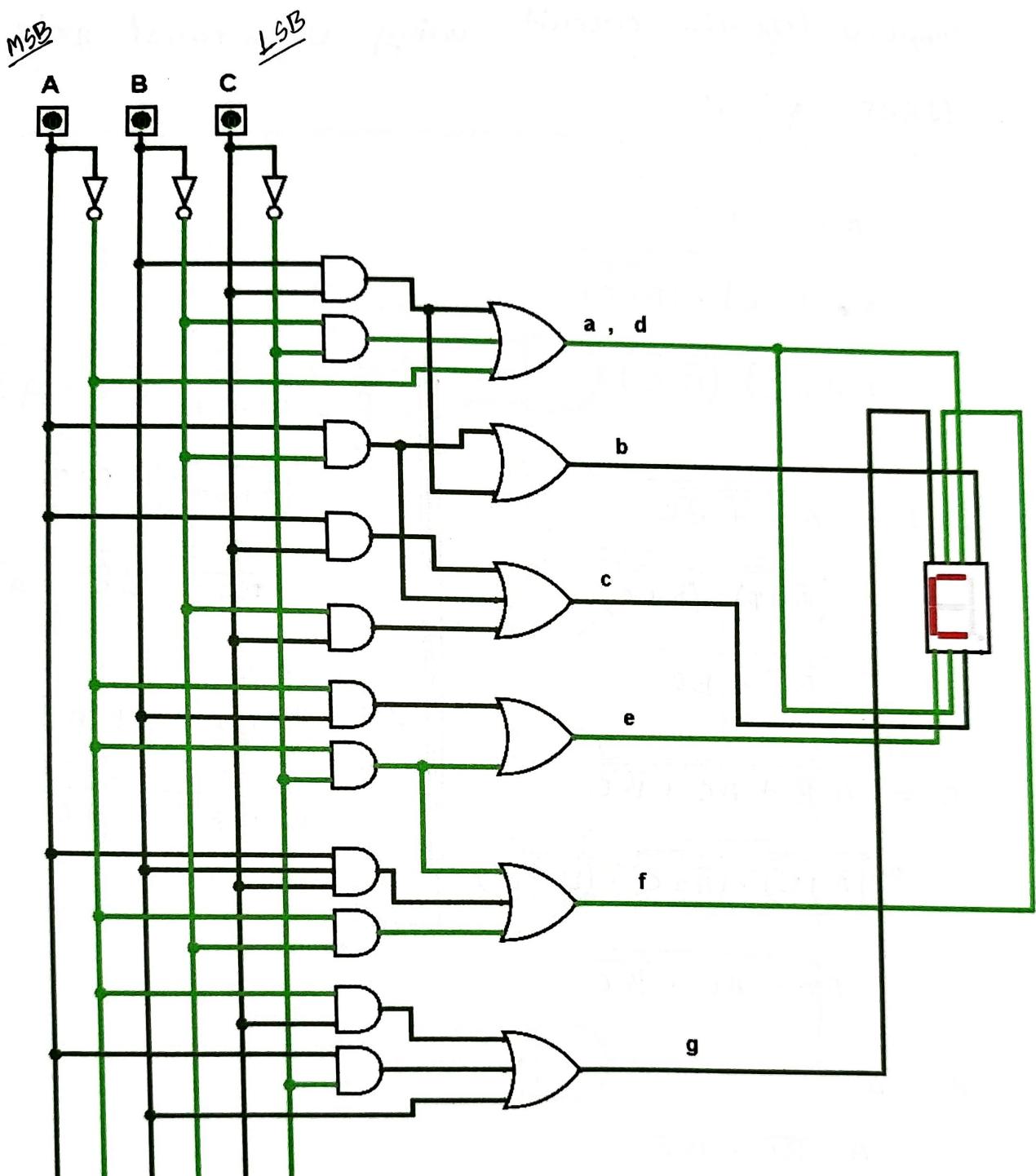

**Figure P.1: Implementation of 7 segment circuit using Basic GATES**

Implementing the circuit using universal gate

NAND gates:

$$a = \overline{\overline{\overline{A} + BC + \overline{B} \cdot \overline{C}}}$$

$$= \overline{A} \cdot \overline{(\overline{B} + \overline{C})} \cdot \overline{(B + C)}$$

$$= \overline{A} \cdot (\overline{B} \cdot \overline{C}) \cdot (\overline{B} \cdot \overline{C})$$

$\oplus$

$$b = \overline{\overline{A \overline{B} + BC}}$$

$$= \overline{(\overline{A} + B)} \cdot \overline{(\overline{B} + \overline{C})}$$

$$= \overline{A \overline{B}} \cdot \overline{B \overline{C}}$$

$$c = \overline{\overline{A \overline{B} + AC + \overline{B} C}}$$

$$= \overline{(\overline{A} + B)} \cdot \overline{(\overline{A} + \overline{C})} \cdot \overline{(B + \overline{C})}$$

$$= \overline{A \overline{B}} \cdot \overline{AC} \cdot \overline{B C}$$


$$d = a$$

$$= \overline{A \cdot \overline{BC} \cdot \overline{B \overline{C}}}$$


$$e = \overline{\overline{AB + \overline{A} \overline{C}}}$$

$$= \overline{A + \overline{B}} \cdot \overline{A + \overline{C}}$$

$$= \overline{AB} \cdot \overline{AC}$$

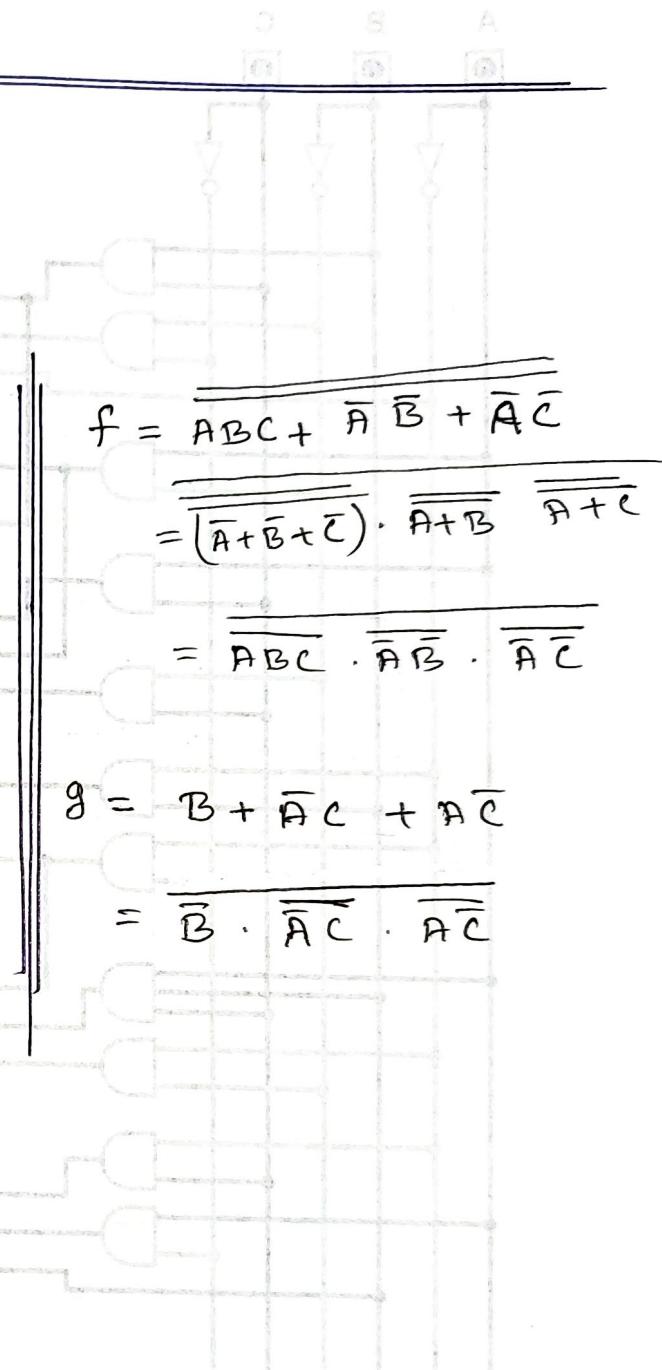

(P-5)

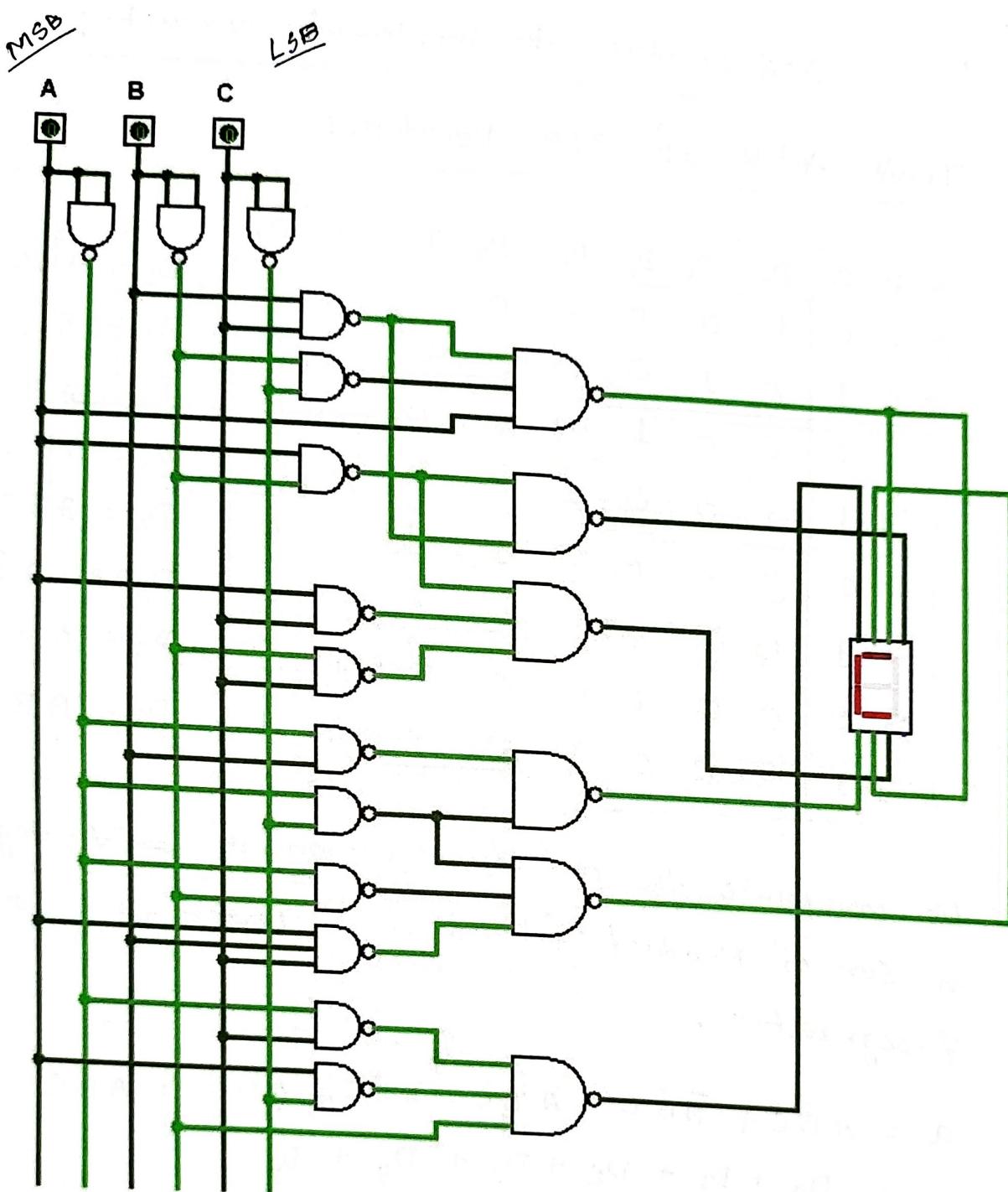

**Figure P.2:** Implementation of 7 segment circuit using Universal GATE  
(NAND GATE)

P-6

Using 3:8 Decoders to implement circuit:

Truth table of 3:8 Decoders:

A	B	C	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

$$D_0 = \bar{A}\bar{B}\bar{C}$$

$$D_1 = \bar{A}\bar{B}C$$

$$D_2 = \bar{A}BC$$

$$D_3 = \bar{A}BC$$

$$D_4 = A\bar{B}\bar{C}$$

$$D_5 = A\bar{B}C$$

$$D_6 = ABC$$

$$D_7 = ABC$$

We can write the outputs equation of 7-segment in sum of Product form, from Truth table of 7-segment.

$$\begin{aligned} a &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC \\ &= D_0 + D_1 + D_2 + D_3 + D_4 + D_7 \end{aligned}$$

$$b = \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + ABC = D_3 + D_4 + D_5 + D_7$$

$$c = \bar{A}\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C + ABC = D_1 + D_4 + D_5 + D_7$$

$$d = a = D_0 + D_1 + D_2 + D_3 + D_4 + D_7$$

$$e = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}BC = D_0 + D_2 + D_3$$

$$f = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + ABC = D_0 + D_1 + D_2 + D_7$$

$$g = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + AB\bar{C} = D_1 + D_2 + D_3 + D_4 + D_6 + D_7$$

$$= D_1 + D_2 + D_3 + D_4 + D_6 + D_7$$

(P-7)

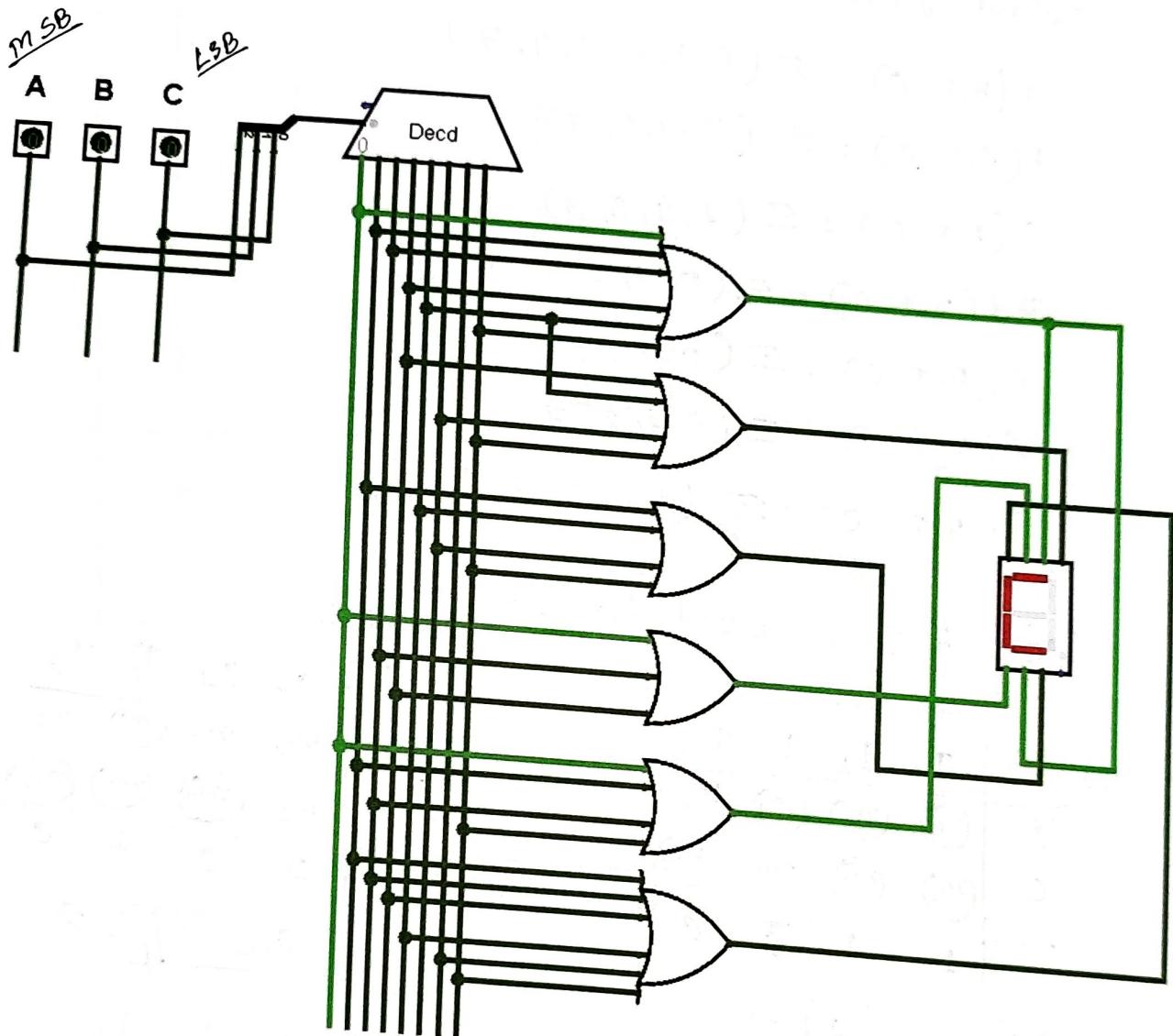


Figure P.3: Implementation of 7 segment circuit using 3 to 8 Line Decoder

P-8

Implementing  $\Phi$  circuit using  $8 \times 1$  MUX:

Output functions are,

$$a(A, B, C) = \Sigma(0, 1, 2, 3, 4, 7)$$

$$b(A, B, C) = \Sigma(3, 4, 5, 7)$$

$$c(A, B, C) = \Sigma(1, 4, 5, 7)$$

$$d(A, B, C) = \Sigma(0, 1, 2, 3, 4, 7)$$

$$e(A, B, C) = \Sigma(0, 2, 3)$$

$$f(A, B, C) = \Sigma(0, 1, 2, 7)$$

$$g(A, B, C) = \Sigma(1, 2, 3, 4, 6, 7)$$

Let, A, B be select bit for all.

	$I_0$	$I_1$	$I_2$	$I_3$
$\bar{C}$	$m_0$	$m_2$	$m_4$	$m_6$
C	$m_1$	$m_3$	$m_5$	$m_7$
	1	1	$\bar{C}$	C

for a, d

	$I_0$	$I_1$	$I_2$	$I_3$
$\bar{C}$	$m_0$	$m_2$	$m_4$	$m_6$
C	$m_1$	$m_3$	$m_5$	$m_7$

for c

	$I_0$	$I_1$	$I_2$	$I_3$
$\bar{C}$	$m_0$	$m_2$	$m_4$	$m_6$
C	$m_1$	$m_3$	$m_5$	$m_7$

for f

	$I_0$	$I_1$	$I_2$	$I_3$
$\bar{C}$	$m_0$	$m_2$	$m_4$	$m_6$
C	$m_1$	$m_3$	$m_5$	$m_7$

for b


	$I_0$	$I_1$	$I_2$	$I_3$
$\bar{C}$	$m_0$	$m_2$	$m_4$	$m_6$
C	$m_1$	$m_3$	$m_5$	$m_7$

for e

	$I_0$	$I_1$	$I_2$	$I_3$
$\bar{C}$	$m_0$	$m_2$	$m_4$	$m_6$
C	$m_1$	$m_3$	$m_5$	$m_7$

for g

(P-9)

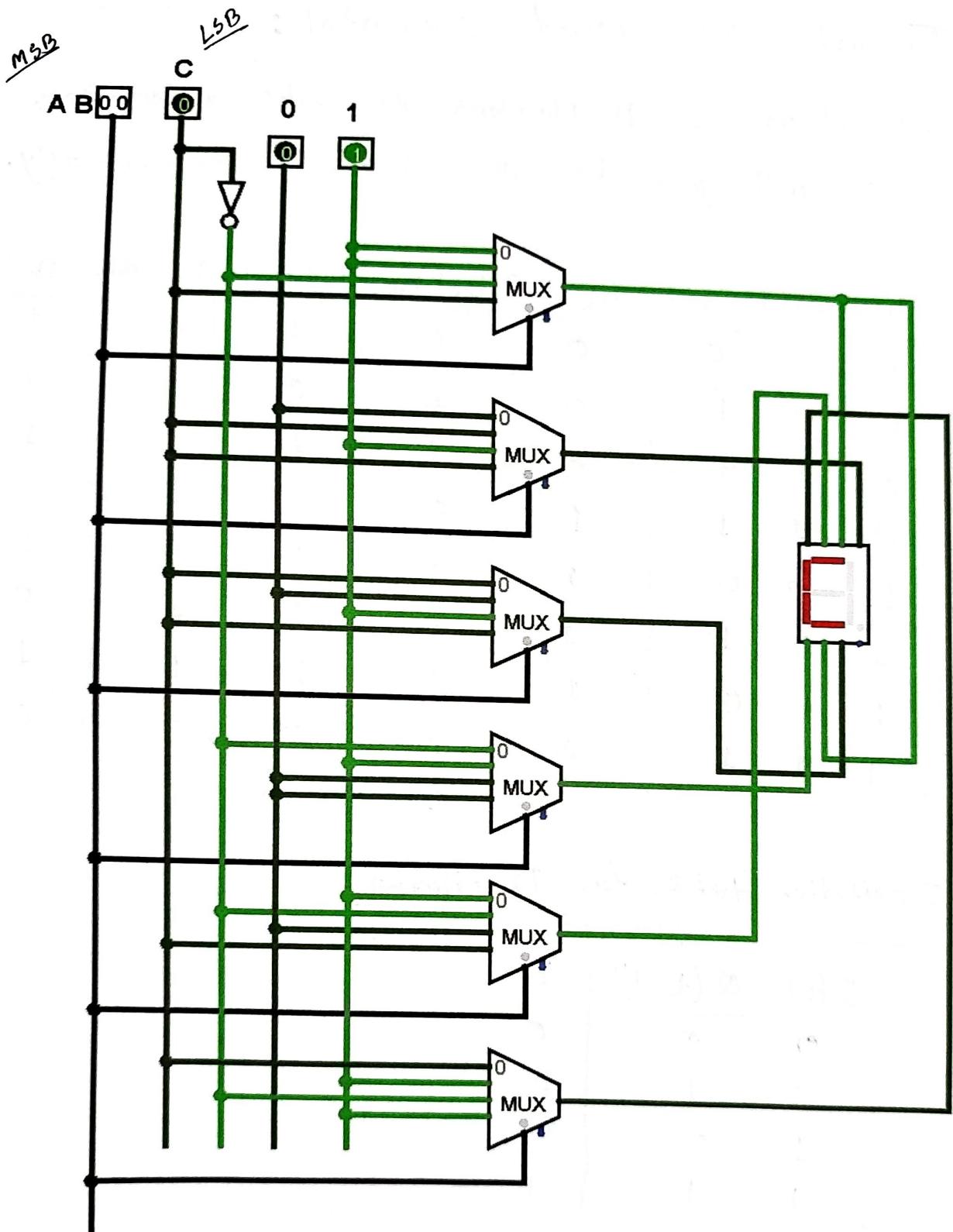

**Figure P.4: Implementation of 7 segment circuit using 4:1 Multiplexers**

To make the circuit sequential :

We will use 3 D-flipflops to make a counter which will generate the inputs sequentially.

A(t)	B(t)	C(t)	A(t+1)	B(t+1)	C(t+1)	D <sub>A</sub>	D <sub>B</sub>	D <sub>C</sub>
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0

Excitation table for D-flipflop :

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

After using this counter, we can see the output "CSE231-9" sequentially.

K-maps :for  $D_A$ :

			$B(t)$
		$A(t)$	
			1
	1	1	1
1		1	1
1	1		1

$C(t)$

$$D_A = A(t) \cdot \bar{B}(t) + A(t) \cdot \bar{C}(t) \\ + \bar{A}(t) \cdot B(t) \cdot C(t)$$

for  $D_B$ :

			$B(t)$
		$A(t)$	
			1
	1	1	1
1		1	1
1	1		1

$C(t)$

$$D_B = \bar{B}(t) \cdot C(t) + B(t) \cdot \bar{C}(t)$$

			$B(t)$
		$A(t)$	
			1
	1		1
1			1
1	1		1

$C(t)$

$$D_C = \bar{C}(t)$$

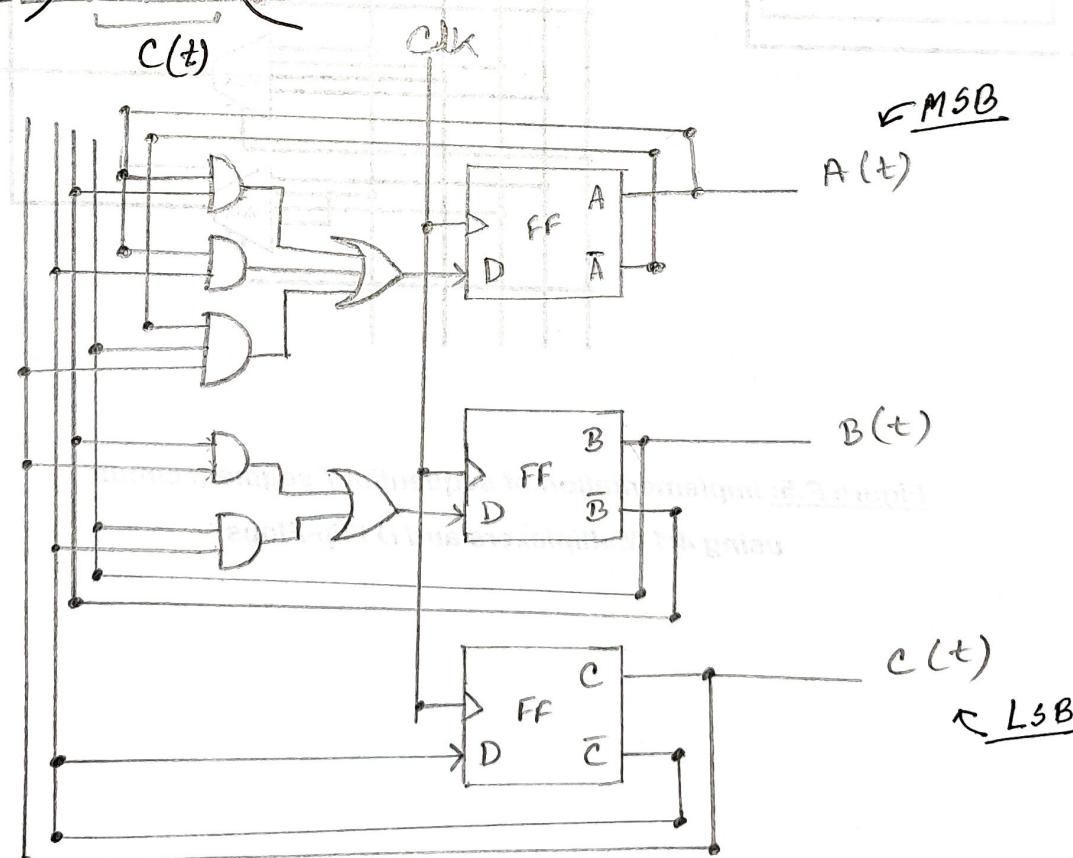
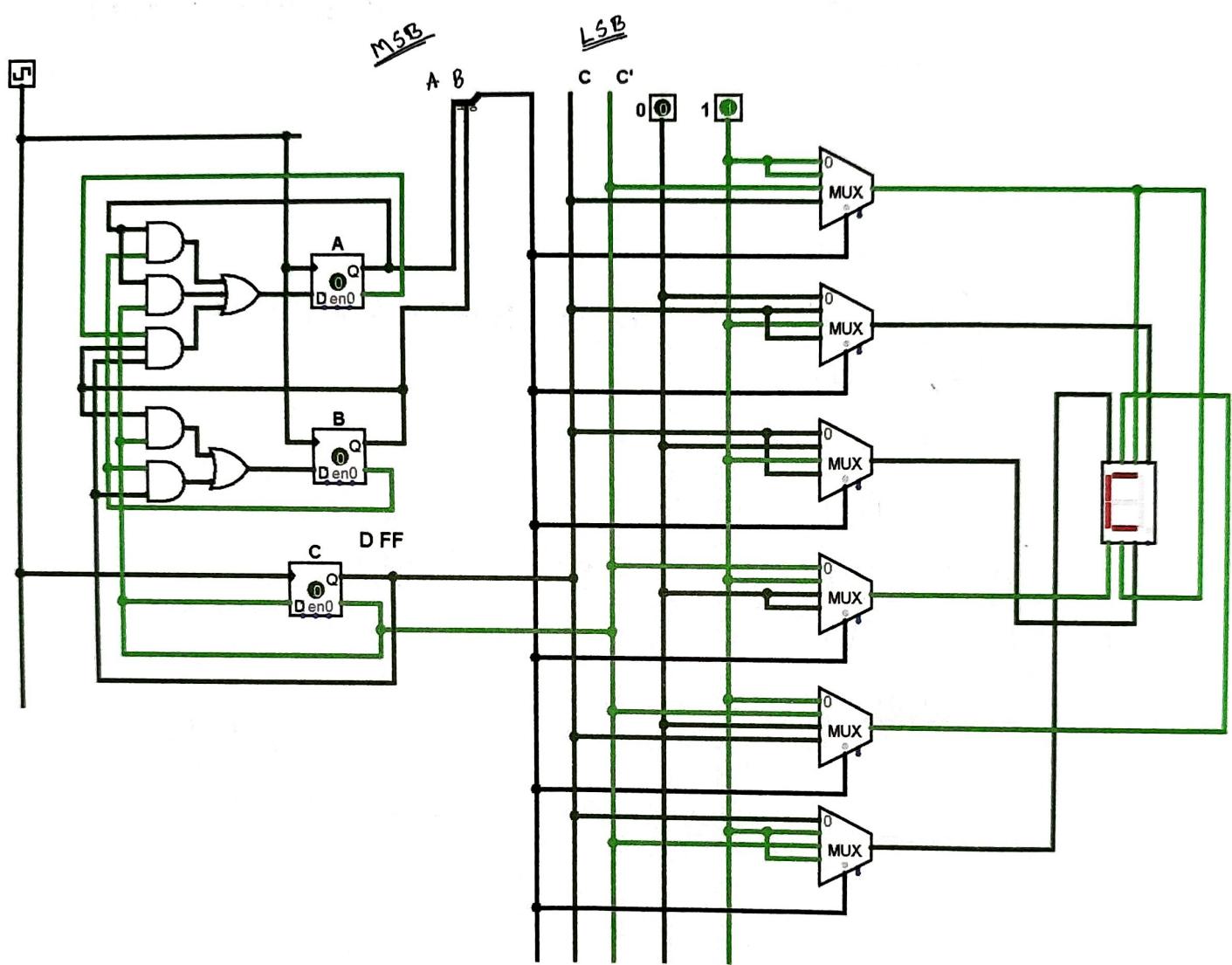
 $\leftarrow$  MSB $A(t)$  $B(t)$  $C(t)$  $\leftarrow$  LSB

Fig: Counters for 7 segment sequential circuit



**Figure P.5: Implementation of sequential 7 segment circuit  
using 4:1 Multiplexers and D Flip-Flops**